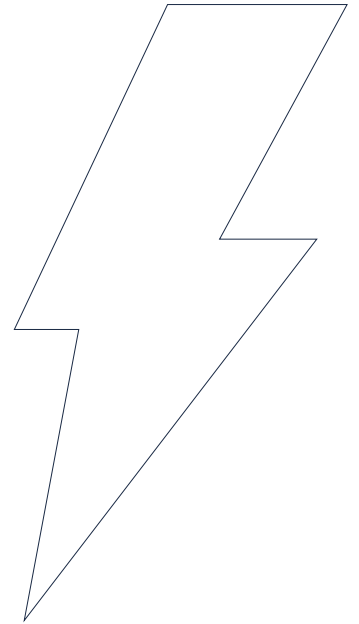




Best Practices in Electrical Integration of the FlexiForce™ Sensor



Thin, customizable FlexiForce sensors measure normal compressive forces in your device. While every application is unique, there are some universal considerations and general best practices to consider to achieve optimal performance of the FlexiForce™ sensor in your application.

This document is intended to illustrate electrical design concepts to consider while integrating FlexiForce sensors into a product or device. Refer to the “FlexiForce Integration Guide” for more detailed information, and contact Tekscan for recommendations on electrical design specific to your application.

Note: The specific circuits in this document are not the only circuit designs that can be used with FlexiForce sensors. We encourage you to engage with our Applications Engineering team early in your process.



Contents


- 1 Fundamentals of a FlexiForce sensors**
page 3
- 2 Circuit Selection**
pages 4-7
 - Inverting Op-Amp Circuit
 - Non-Inverting Op-Amp Circuit
 - Voltage Divider Circuit
- 3 Develop Sensitivity Adjustment and Calibration Procedure**
page 8
- 4 Calibration Walk-Through Example**
page 9
- 5 Additional Resources**
page 10
- 6 FlexiForce OEM Development Products**
page 11

1

Fundamentals of a Flexiforce™ Sensor

A FlexiForce sensor behaves as a variable resistor greater than 2 M Ω when unloaded and dropping about 25K Ω when it is subjected to its peak measurement load.

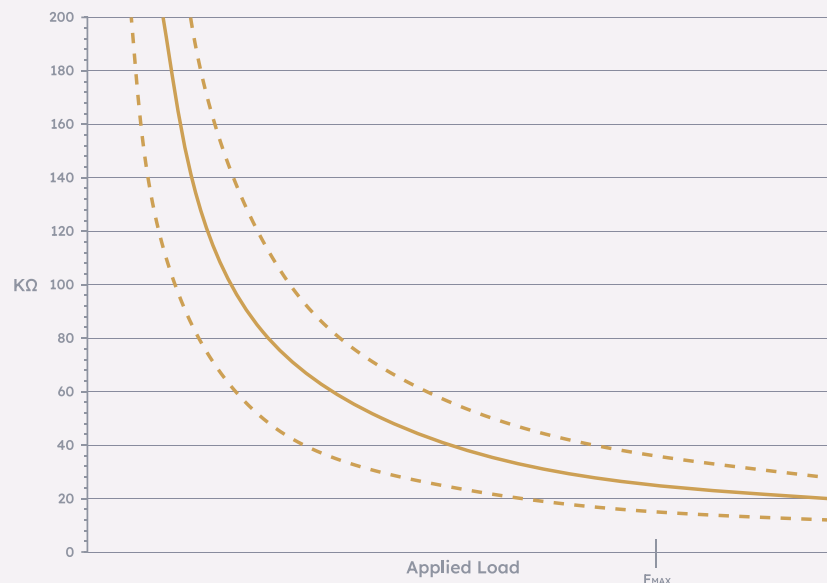The solid line represents the target force to resistance correlation. The two dotted lines represent the potential variance of this relationship. The F_{MAX} location represents the range of resistance values where the curve of a sensor may land.



This document will cover some recommended circuits and settings to drive repeatable linear output from FlexiForce Sensors.

- Mechanical design heavily influences sensor behavior and should be completed before finalizing circuit design. Consult the “**Mechanical Best Practices Guide**” documentation regarding effects of:

- Interface material
- Load concentration
- Environment

- Lower reference voltages (0.25-0.75V) reduce power consumption, provide more force range and resolution adjustability


**Additional
Recommendations**

2


Circuit Selection

Tekscan recommends choosing from one of three circuits to operate FlexiForce sensors.


Inverting Op-Amp Circuit

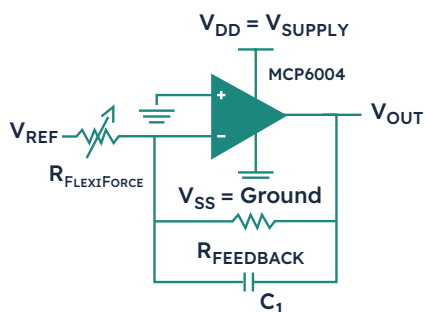

Non-Inverting Op-Amp Circuit

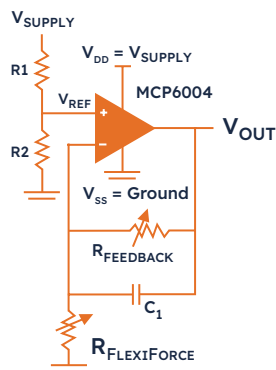

Voltage Divider

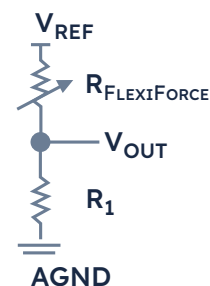

Usage

Best for measuring wide dynamic ranges

Good for measuring smaller dynamic ranges

Best for basic applications measuring threshold value

Linearity



Dynamic Range



Noise Suppression



of Power Supplies

2

1

1

Cost

\$\$\$

\$\$

\$>


Performance Notes

Very linear through origin

Very linear through offset, less dynamic range than Inv. Op-Amp

Not linear. Output will decrease at higher loads

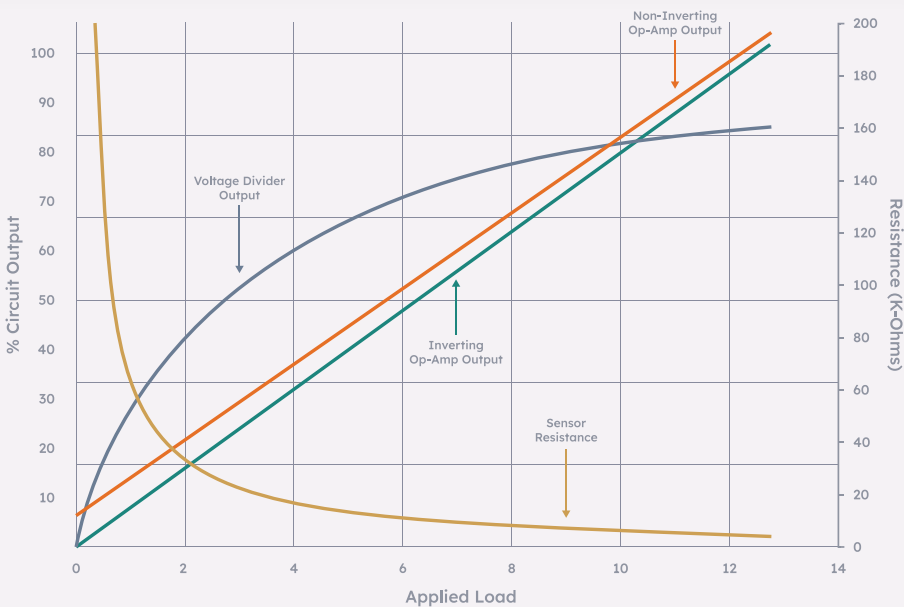
Digital output of 3 circuits under same load conditions





Inverting Op-Amp Circuit

$R_{\text{FEEDBACK}} = 20\text{k}\Omega$
(100k Ω Potentiometer can be used for adjustable sensitivity)
 $C_1 = 47\text{pF}$

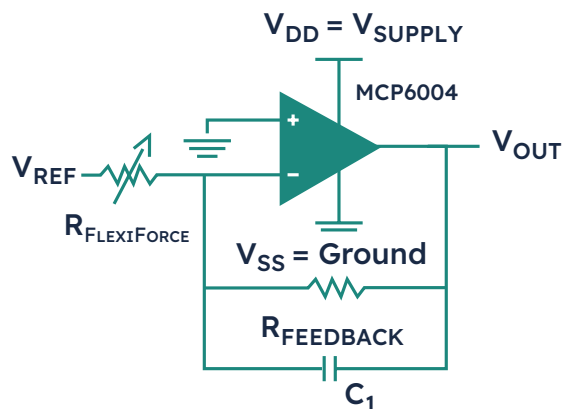Note: Potentiometer and Capacitor values are general recommendations. Testing should be performed to determine optimal settings.




Reference Voltages

	 Duty Cycle	 DC
Notes	Ideal for sensor performance and reduced power consumption	Can stress sensor over time – not recommended for continuous load applications
V_{REF} Max	5V	1V
V_{REF} Ideal	0.25-0.75V	
Max Duty Cycle	20%	N/A
Max Current	2.5mA	


Adjusting Force Sensitivity

To address sensor variance, the output to load correlation can be adjusted by:

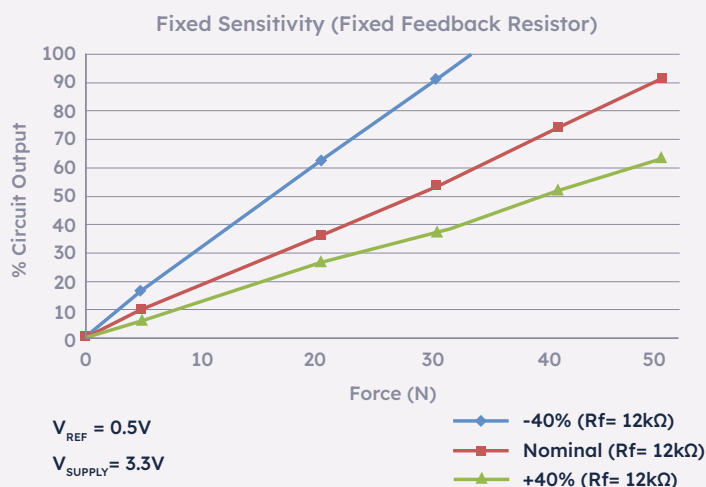- The feedback resistor can be configured with an analog or digital potentiometer
- The reference voltage can be adjusted with a voltage divider or Digital to Analog Converter (DAC)



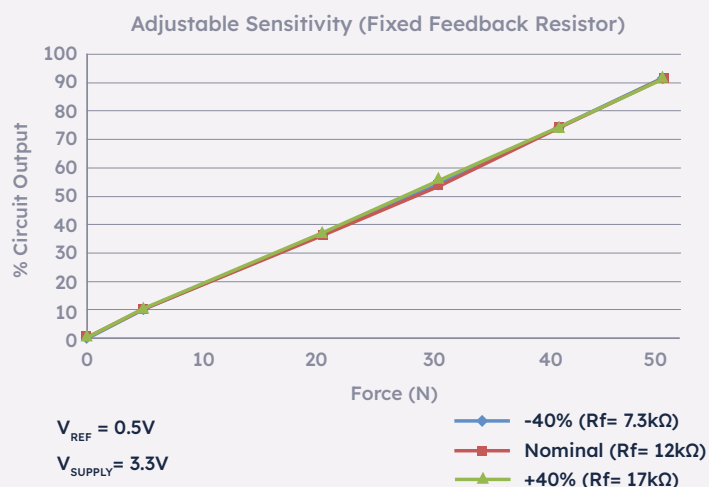More sensitive sensors saturate before max force.



All sensors operate within dynamic force range.

Unlike a Non-Inverting Op-Amp, this will NOT affect the dynamic Range

Consult the “FlexiForce Integration Guide” for more models and Graphs



Download




Non-Inverting Op-Amp Circuit

$R_{\text{FEEDBACK}} = 80\Omega$

(100K Ω Potentiometer can be used for adjustable sensitivity)

$C_1 = 47\text{pF}$ $R_1 = 20\text{K}\Omega$ $R_2 = 80\text{K}\Omega$

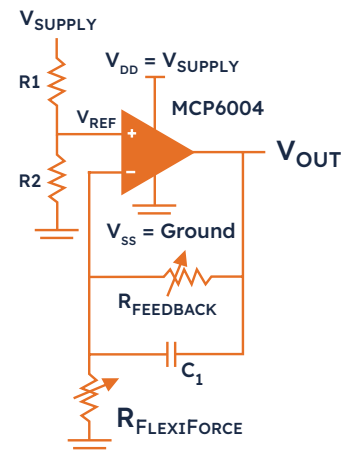Note: Potentiometer and Capacitor values are general recommendations. Testing should be performed to determine optimal settings.




Reference Voltages

	Duty Cycle	DC
Notes	Ideal for sensor performance and reduced power consumption	Can stress sensor over time – not recommended for continuous load applications
V_{REF} Max		1V
V_{REF} Ideal		0.25-0.75V
Max Duty Cycle	20%	N/A
Max Current		2.5mA


Adjusting Force Sensitivity

To address sensor variance, the output to load correlation can be adjusted by:

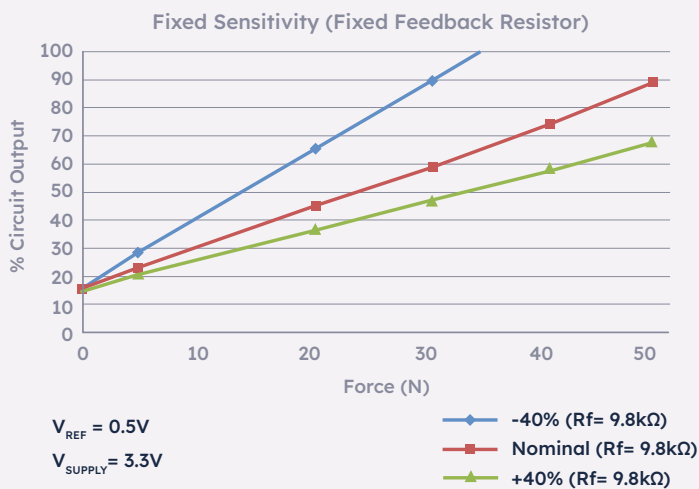- The feedback resistor can be configured with an analog or digital potentiometer
- The reference voltage can be adjusted with a voltage divider or Digital to Analog Converter (DAC)



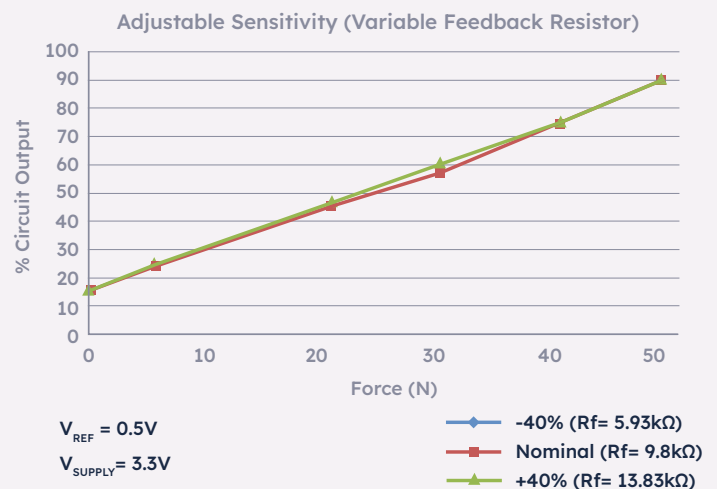More sensitive sensors saturate before max force.



All sensors operate within dynamic force range.

Increasing V_{REF} on a Non-Inverting Op-Amp will reduce the dynamic range of the system

Consult the “FlexiForce Integration Guide” for more models and Graphs



Download




Voltage Divider



$R_1 = 100K\ \Omega$

(100K Ω Potentiometer can be used for adjustable sensitivity)

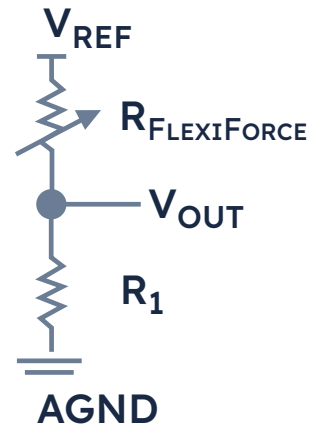Note: Potentiometer value is a general recommendation. Testing should be performed to determine optimal settings




Reference Voltages

	 Duty Cycle	 DC
Notes	Ideal for sensor performance and reduced power consumption	Can stress sensor over time – not recommended for continuous load applications
V_{REF} Max	5V	1V
V_{REF} Ideal	0.25-0.75V	
Max Duty Cycle	20%	N/A
Max Current	2.5mA	

Adjusting Force Sensitivity

To address sensor variance, the output to load correlation can be adjusted by:

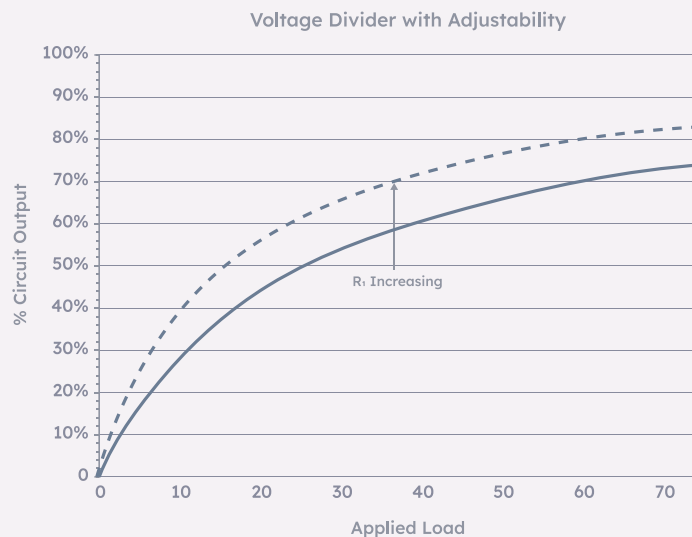- The R_1 can be configured with an analog or digital potentiometer
- The reference voltage can be adjusted with a Digital to Analog Converter (DAC)



Consult the “FlexiForce Integration Guide” for more models and Graphs



Download



3

Develop Sensitivity Adjustment and Calibration Procedure

Sensitivity adjustment:

Use the circuit's sensitivity adjustment method to set the output of the circuit to 80%-90% of full-scale at maximum applied force.

Calibration

Apply known force to the sensor to correlate voltage output to engineering units (lbs, N, psi, etc). Because of the inherent part-to-part variation in FlexiForce sensors, independent/individual sensor calibration is crucial for achieving accurate results.

Before Calibration

- 1 Fully assemble device to be in the same state or as similar as possible, to when it will be used in the field
- 2 If possible, condition the sensor. We generally recommend loading the sensor to 120% of maximum expected force and cycling 3-5 times for 10 seconds at a time

- Adjusting the sensitivity of the circuit to max output at 120% max load, or 80-90% output at 100% load allows some overhead for spikes in force/pressure. This process ensures that the circuit does not saturate before your maximum expected force. Using one of the circuits and a circuit design process previously described in Sections 1 & 2 will help ensure the circuit sensitivity can be properly adjusted throughout the range of possible sensor resistances.
- 3

During Calibration

Use Completed Assembly, Or As Close to Completed As Possible

Use Force Levels Within The Expected Application Force Range

Use The Same Load Duration As Expected During The Application


4

Calibration Walk-Through Example

Condition The Sensor (Recommended)

Conditioning is only required prior to factory calibration.

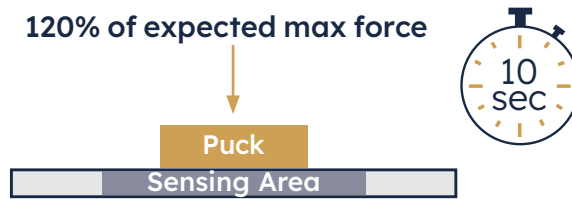Apply & remove force at 120% of the expected max force 3-5 times, 10 seconds each time.



Adjust Circuit Sensitivity To 90% Of Circuit's Max Output

Apply max expected force. Adjust sensitivity so that output is 90% of the circuit's maximum output. Remove force

Refer to Section 2 of this document, or the "FlexiForce Integration Guide" for sensitivity adjustment methods.



Note: In this example, the circuit saturates at 3.3V. Max expected load is 44.4 N (10 lbs).

Plot Force VS Recorded Output


We generally recommend a two-to-three point calibration. First record the circuit output with the sensor unloaded, then:

1. Apply a low calibration point of 10% max load
2. (Optional) Apply a mid calibration point at 50% max load, if desired
3. Apply a high calibration point at 100% of max load

Record circuit output at each load.

In this example, we are recording circuit output with the sensor unloaded, then applying 4.4 N, 22.2 N, and 44.4 N (1 lb, 5 lbs, and 10 lbs, respectively) sequentially at the expected loading time interval.

Force (N (lbs))	Circuit Output (V)
0 (0)	0.51
4.4 (1)	0.75
22.2 (5)	1.70
44.4 (10)	2.96

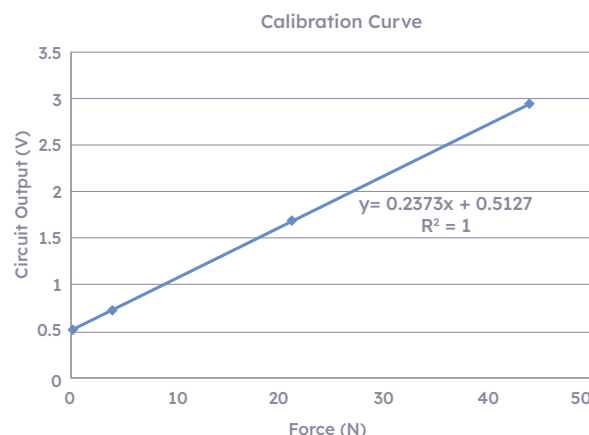


Note: Calibration can also be carried out as a function of ADC counts if ADC is being used.

Best Practices in Mechanical Integration

The complete “**Best Practices in Mechanical Integration**” guide provides key recommendations to consider during the prototyping phase of your OEM project. This includes:

- Applying load concentrators to ensure even loading
- Recommendations to minimize shear force and preserve sensor sensitivity
- Methods for mounting the sensor, and more!

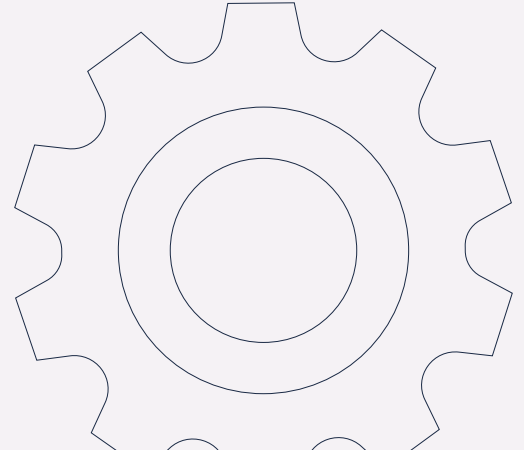[Download](#)

FlexiForce Integration Guide

For in-depth OEM integration recommendations, download the complete “**FlexiForce Integration Guide**.” This guide is intended to help you optimize design, reduce costs, and streamline the overall sensor design & embedding process from prototype to production.

The “FlexiForce Integration Guide” includes additional mechanical considerations to help with your OEM project, including:



- Characterizing sensor performance
- Soldering
- Effects of temperature on circuit and calibration
- Sensor/circuit duty cycle
- Design walk-thru examples, and more!

[Download](#)

FlexiForce OEM Development Products

Tekscan offers two FlexiForce Integration Kits to help engineers test and evaluate FlexiForce Sensors for their embedded product or device. These include:

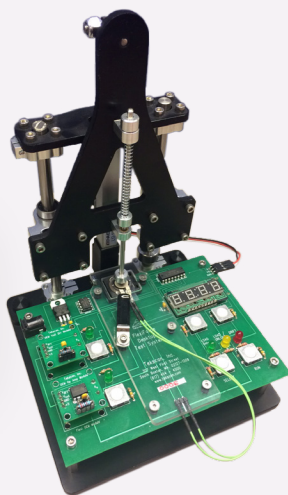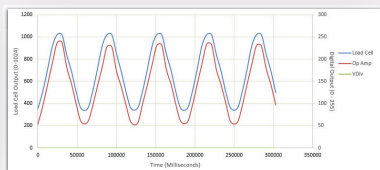
The FlexiForce Sensor Characterization Kit



- An all-in-one testing fixture to help collect baseline sensor performance in a controlled loading environment
- Test interfacing materials with pre-programmed loading profiles in open-source software:
 - Linearity
 - Hysteresis
 - Drift
 - Repeatability
- Use with any [FlexiForce Standard Sensor](#) model, except the A101

[Learn More](#) →

The FlexiForce Prototyping Kit

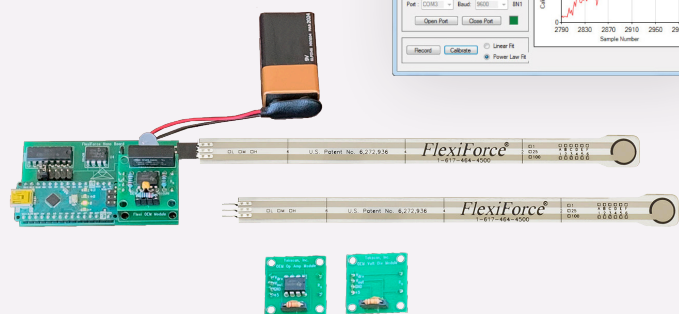

- A compact, plug & play kit to help engineers and designers progress smoothly through later integration phases
 - Begin collecting data in minutes!
- Test with different circuitry and make sensitivity adjustments with ease
- Use with any [FlexiForce Standard Sensor](#) model, except the A101

[Learn More](#) →

What's Next?

Are you considering embedding a FlexiForce sensor into your product? Contact our Application Engineering team today to help bring your OEM project to life.



617.464.4283
1.800.248.3669

info@tekscan.com
tekscan.com/flexiforce